
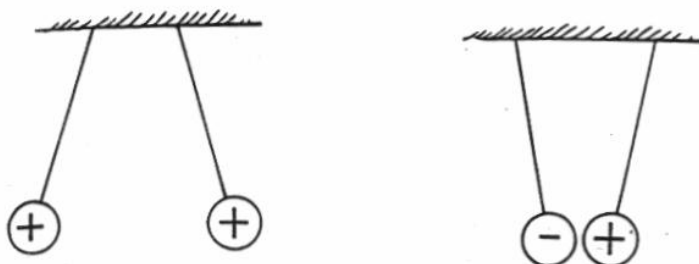


ELECTRICAL CHARGES

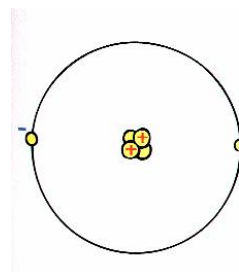
- **Static electricity** is the *accumulation of electric charges* on an object.
- Electric **charges** are caused by an *imbalance* between **positive** (protons) and **negative** (electrons) particles in matter.
- **Like** charges *repel* each other, while **unlike** charges *attract*.



- Presence of electrical charges can be detected by the use of an **electroscope**.


Neutral objects can be charged in two ways:

- Charging of neutral objects through **contact** is called **conduction**.
- Charging of neutral objects **without** direct **contact** is called **induction**.
- **Conductors** are substances that **allow** electrons to **move easily** through them. **Metals** are examples of good conductors.
- **Insulators** are substances that **don't allow** electrons to **move easily** through them. **Plastics, wood and glass** are good insulators.

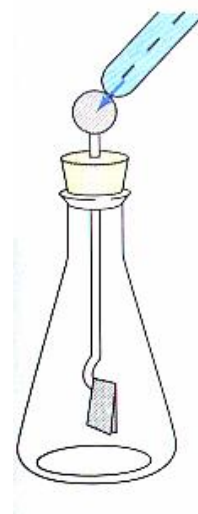

ELECTRIC FORCES

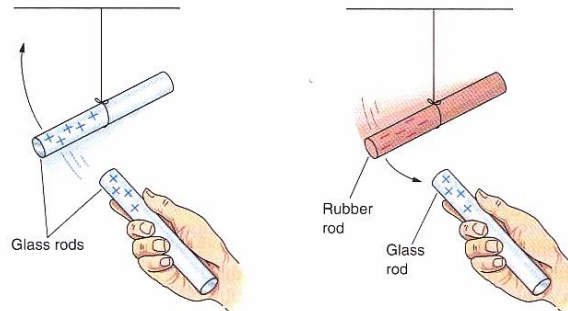- *Repulsions* and *attractions* caused by electrical charges are *forces*.



- The magnitude of the electric forces is described by *Coulomb's Law*:

$$F = k \frac{q_1 q_2}{r^2}$$

where,

F = force of attraction or repulsion

q_1 and q_2 = electric charges

r = distance between the charges

k = the Coulomb's constant

Examples:

Two positive charges are a distance of 2 cm from one another. If they are moved to a distance of 1 cm, the force between them

- A) increases 2 times
- B) decreases 2 times
- C) increases 4 times
- D) decreases 4 times

CURRENT / VOLTAGE / RESISTANCE

Current:



- *Motion* of electric *charges* causes electric *current*.
- *Rate of flow* of electric charges is measured as *electric current*.

$$\text{current} = \frac{\text{charge}}{\text{time}} = \frac{q}{t}$$

- Electric current is measured as *amperes*.

Voltage:


- When two charges are brought together or separated from each other, *work* must be done to overcome the *forces between them*.
- The work thus done increases the *electric potential energy* of the charges.
- When the charge is released, the electrical *PE is converted to KE*.
- The *electrical potential difference* is what is measured as *voltage (V)*.

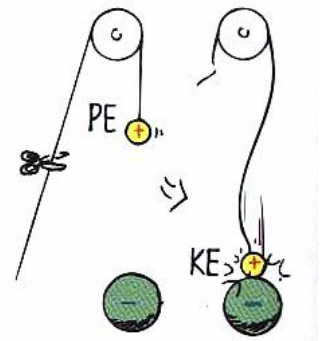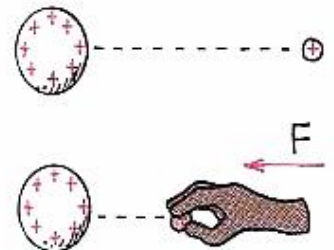Resistance


- When current flows through a conducting material, it meets some opposition to its flow due to collisions within the material.
- This property is called *resistance (R)* and is measured in *ohms (Ω)*.

ELECTRIC CIRCUIT & WATER ANALOGY

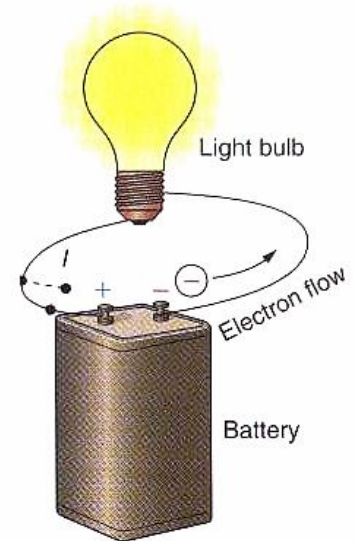- In the electric circuit, the battery provides the voltage, current flows through the wire and the bulb provides the resistance to flow of electrons.



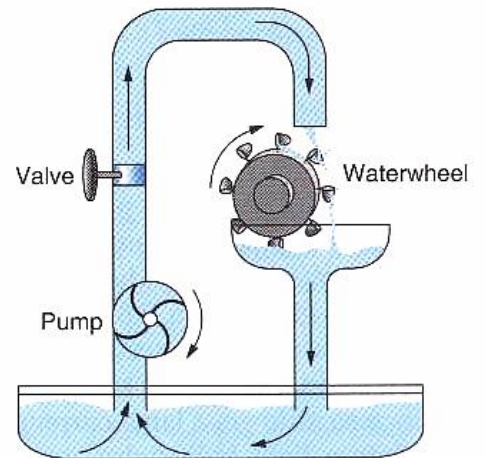- In the water circuit, the pump is analogous to the battery, the pipe represents the wire carrying water flow, and the water wheel provides resistance to flow of water.



OHM'S LAW

- The relationship between *voltage*, *current* and *resistance* in a circuit is called Ohm's Law and is described as follows:

$$\text{Voltage} = \text{Current} \times \text{Resistance}$$

$$(\text{volts}) = (\text{amperes}) \times (\text{ohms})$$

$$V = I R$$

Examples:

1. A toaster with a resistance of 50Ω is connected to a 120 V source. What current flows through the toaster?

$$V =$$

$$R =$$

$$I =$$

2. A 12-V car battery operates a lamp with a current 0.08 amperes. What is the resistance of the lamp?

$$V =$$

$$R =$$

$$I =$$

ELECTRICAL POWER

- **Electrical Power (P)** is the work done by the current against the resistance of the circuit, and can be calculated as follows:

$$P = V I$$

- The **unit** of power is **watts (W)**.

Examples:

1. A color television connected to a 120-V source draws 3.5 A of current. What is the power rating of this TV?

$$V =$$

$$I =$$

$$P =$$

2. A 60-W light bulb is connected to a 120-V power source. Find the current and the resistance of the bulb.

$$V =$$

$$P =$$

$$I =$$

$$R =$$

ELECTRICAL CIRCUITS

- Any **closed path** along which electrons can **flow** is a **circuit**.
- Two types of circuits are possible: **series** & **parallel**.

Series Circuit

- Electric **current** has only **one path of flow** through this circuit.
- The **total resistance** of the circuit is the **sum** of all the **individual resistances**.


$$R_{\text{tot}} = R_1 + R_2 + R_3 + \dots$$

- The **current** through each bulb is the **same**.

$$I = I_1 = I_2 = I_3$$

- The **sum of the voltages** across each bulb equals the source voltage.

$$V_{\text{tot}} = V_1 + V_2 + V_3$$

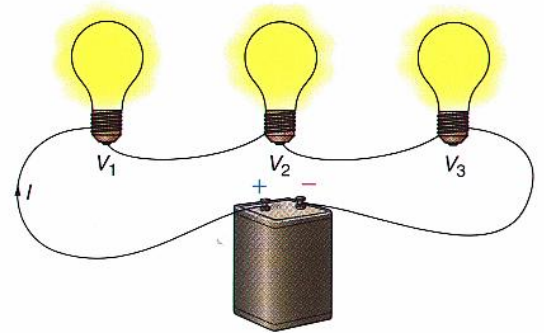Examples:

Three lamps with resistances of 15Ω each are connected to a 72-V power source. What is the current and power through the circuit?

$$R_1 = R_2 = R_3 =$$

$$V =$$


$$I =$$

$$P =$$

ELECTRICAL CIRCUITS

Parallel Circuit

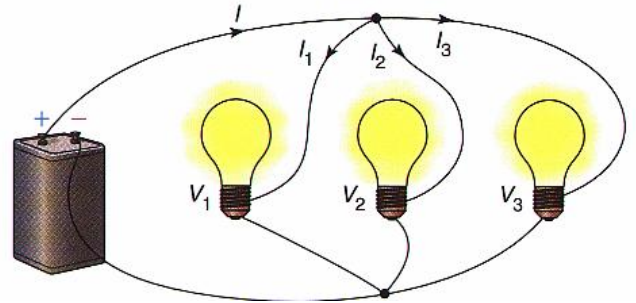- Electric *current* has *more than one path of flow* through this circuit.
- The *total resistance* of the circuit is *less than the smallest* resistance in the circuit.



$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

- The *total current* in the circuit is equal to the *sum of the currents* in its parallel branches.

$$I_{\text{tot}} = I_1 + I_2 + I_3$$

- In this circuit, the *voltage* across each branch is the *same*.

$$V_{\text{tot}} = V_1 = V_2 = V_3$$

Example:

1. Two lamps with resistances of 6Ω and 3Ω respectively are wired in parallel. Calculate the total resistance of this circuit.

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \underline{\hspace{2cm}}$$

2. When three 15Ω lamps are connected in parallel to a 72-V power source, the current through each lamp is 4.8 amperes. What is the total resistance in this circuit?

$$I_{\text{Total}} =$$

$$V =$$


$$R =$$

COMPARING CIRCUITS

- There are several differences in operation between the series and the parallel circuits.


Series Circuit	Parallel Circuit
<ul style="list-style-type: none"> ➤ If <i>one</i> lamp <i>fails</i>, all <i>others stop working</i>. ➤ As <i>more lamps</i> are added to the circuit, total <i>resistance increases</i>, and total <i>current decreases</i>. ➤ As a result the lamps get <i>dimmer</i> as more is added to the circuit. 	<ul style="list-style-type: none"> ➤ If <i>one</i> lamp <i>fails</i>, the <i>others continue to work</i>. ➤ As <i>more lamps</i> are added to the circuit, total <i>resistance decreases</i>, and total <i>current increases</i>. ➤ As a result the circuit can get <i>overheated</i> as more lamps are added to it.

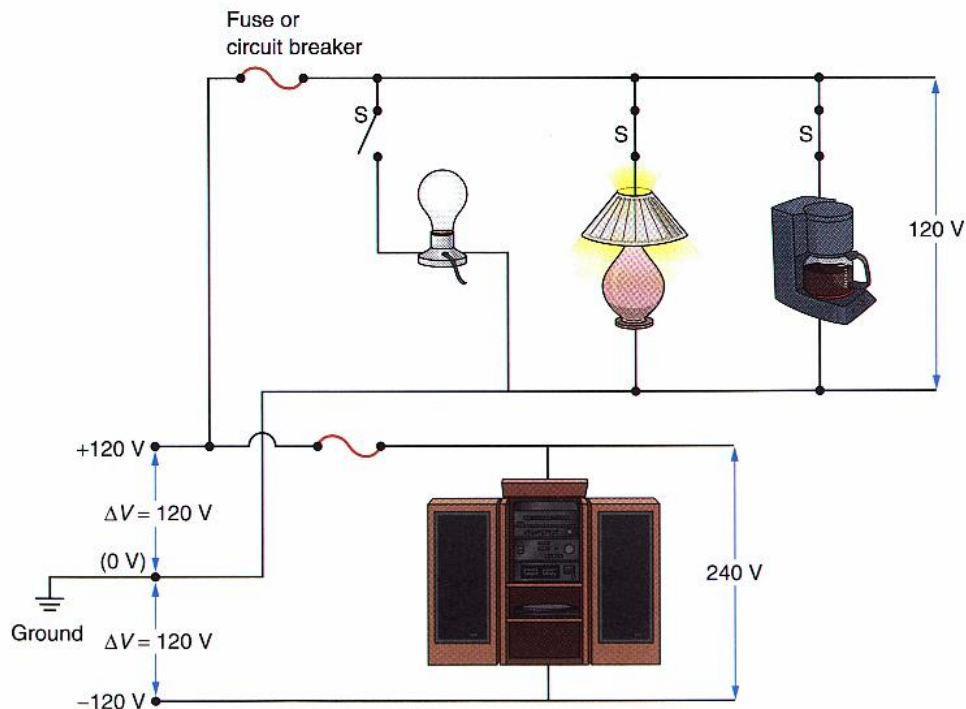- Household circuits are wired in parallel so each appliance can work independently of others.




ELECTRICAL SAFETY

- The damaging effects of **electric shock** on a human body are caused by a **current** and **not by voltage**. The resistance of a human body ranges from 500,000 Ω (dry skin) to about 100 Ω (fully soaked body in salt water).
- For a body to receive shock, there must be a **difference in electric potential** between one part of the body and another.
- That is why a bird can sit on a high voltage wire without any problem, but it had better not reach over and grab a neighboring wire!
- To avoid hazard from an **overheating** circuit, a **fuse** is placed in the circuit. The low melting point of the **fuse wire** causes it to **melt and break** the circuit if the current becomes excessive.
- A dedicated **ground wire** in electrical appliances through a third prong causes the **circuit to be opened** and **electric potential** of the casing to become **zero, avoiding a shock hazard**.

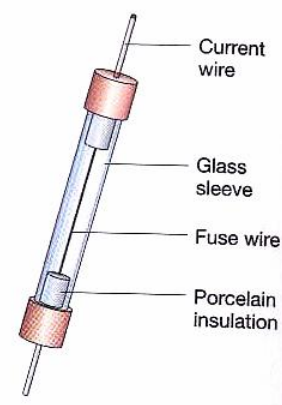


MAGNETIC FORCES & FIELDS

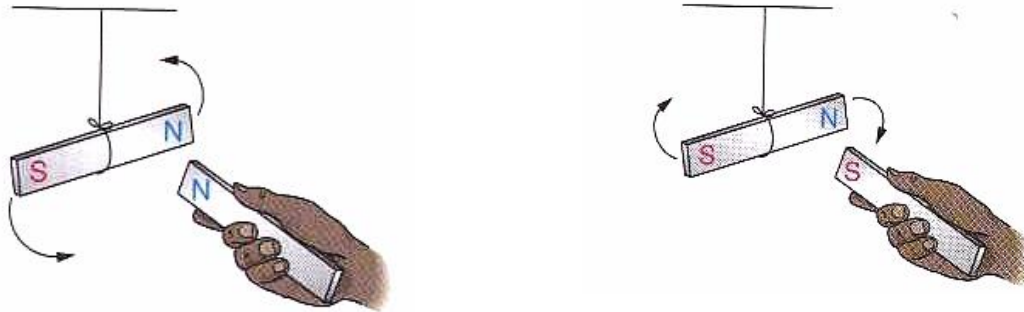- **Magnetic forces** are *similar* to **electric forces**, for they can attract and repel without touching (*action at a distance*).
- Similar to electric charges, *like magnetic poles repel*, while *opposite poles attract*.





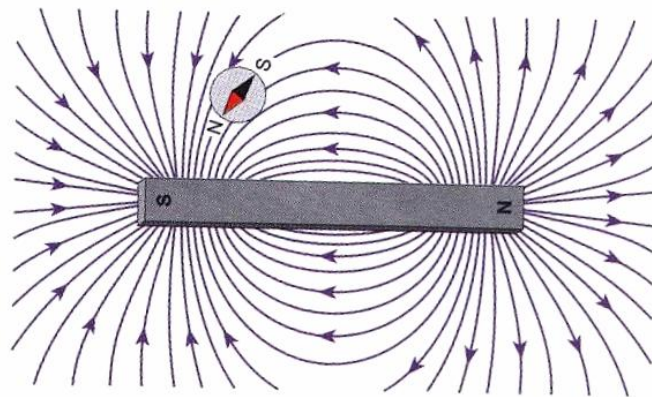- Magnetic *poles cannot be isolated* while *electric charges can*.
- **Magnetic field** is the *area* around a magnet where the **magnetic forces act**, and are concentrated near the poles of a magnet.




MAGNETIC DOMAINS

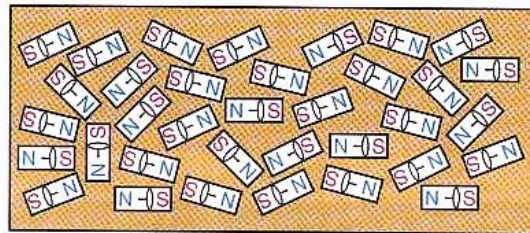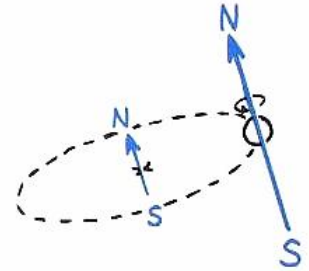- *Magnetic fields* are caused by “*distortions*” in a *moving electric field*.
- These *distortions* are caused by the “*spinning*” and *revolving motion of electrons* in an atom. Each *atom* is therefore a *tiny magnet*.
- A large *cluster of atoms aligned* together give rise to a *magnetic domain*.
- An *unmagnetized* material has *unaligned domains*.



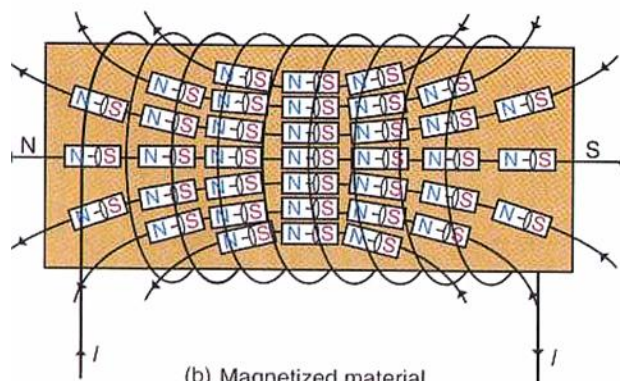(a) Unmagnetized material

- When the domains are *induced into alignment*, *magnetic properties appear*.




(b) Magnetized material


- Domains can be induced into alignment by *rubbing against a strong magnet* or by running *current through a wire* wrapped around a metal.

ELECTROMAGNETISM

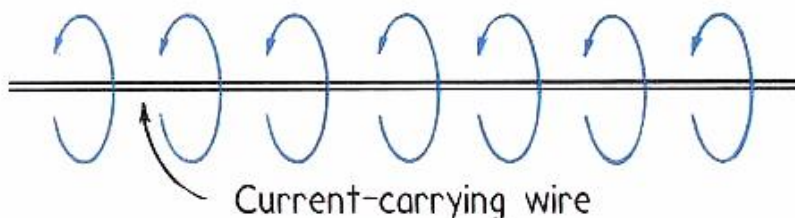- The interaction of *electric and magnetic* effects is called *electromagnetism*.
- An *electric current* produces a *magnetic field perpendicular* to the direction of its movement.



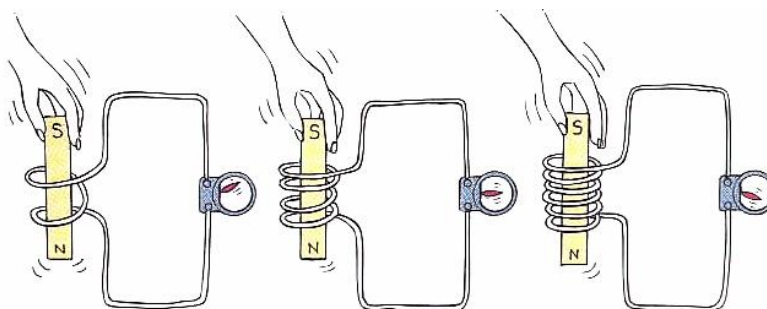
- In early 1800, *Michael Faraday* discovered that an *electric current* could be produced from a *changing magnetic field*.
- *Electromagnetic induction* is the process of creating a current by movement of a magnet through a coil of wire.




- The *amount of current* produced depends on the *number of loops*, the *rate of movement* of the magnet and the *strength of the magnet*.
- Many devices such as a telephone & doorbell use this principle to operate.

APPLICATIONS OF ELECTROMAGNETISM

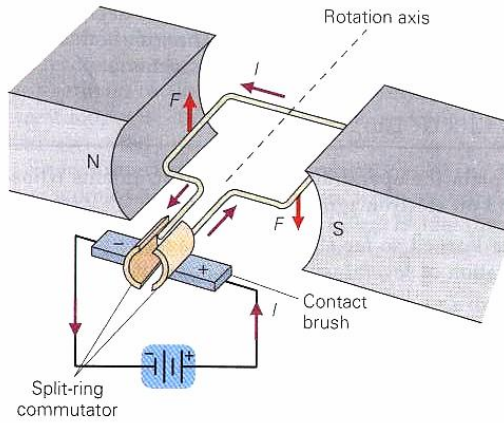- A simple *motor* is an *electromagnet* that converts *electrical energy to mechanical energy*.




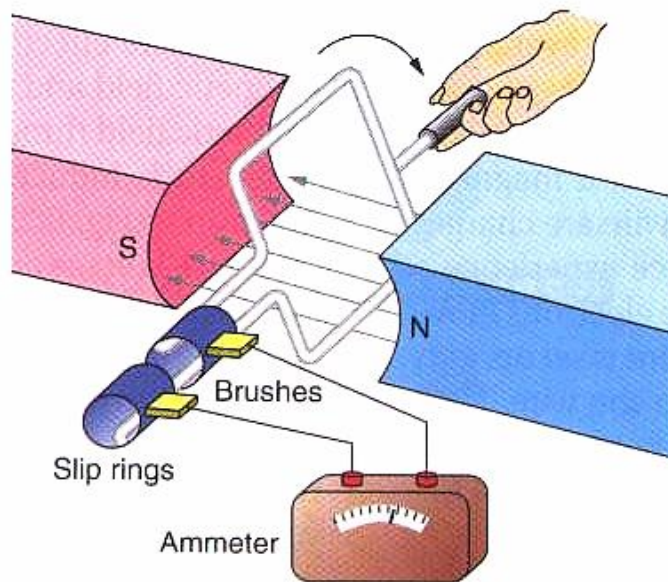- A *generator* converts *mechanical energy to electrical energy*, and uses the principle of *electromagnetic induction*.



TRANSFORMERS

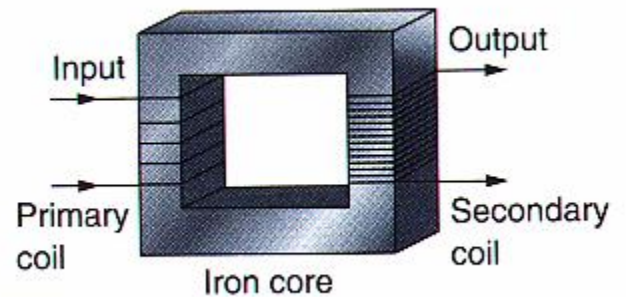- A transformer is used to increase or decrease voltage in a circuit using Faraday's Law.
- A **transformer** consists of two coils of insulated wire wrapped around an iron core.
- **Current** in the primary coil **creates a magnetic field**, which is concentrated by the iron core, and passed through the secondary coil.



- The **magnetic field** in the secondary coil **produces a current** output.
- The **voltage change** in the transformer is based on **Faraday's Law**, and is given by

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \quad \text{or} \quad V_2 = \left(\frac{N_2}{N_1} \right) V_1$$

where,

V_1 = input voltage

N_1 = number of turns in the primary coil

V_2 = output voltage

N_2 = number of turns in the secondary coil

- A transformer that has **more turns** in the **secondary coil** compared to the primary coil is a **step-up** transformer.
- A transformer that has **more turns** in the **primary coil** compared to the secondary coil is a **step-down** transformer.

TRANSFORMERS

- The power output in the primary and secondary coils of a transformer remain the same, therefore

$$P_1 = P_2$$

$$V_1 I_1 = V_2 I_2$$

Examples:

1. A transformer has 500 windings in its primary coil and 25 in its secondary coil. If the input voltage is 4400 V, find the output voltage.

$$N_1 =$$

$$N_2 =$$

$$V_1 =$$

$$V_2 =$$

2. A transformer has 300 turns in its secondary and 50 turns in its primary coil. The input voltage is 12 V. If 3.0 A flows in the primary coil, find the voltage and current in the secondary coil?

$$N_1 =$$

$$N_2 =$$

$$V_1 =$$

$$I_1 =$$

$$V_2 =$$

$$I_2 =$$